

Predict if the following circuits will light. Try testing your prediction using real light bulbs, batteries and wire and then look at the electricity book.

